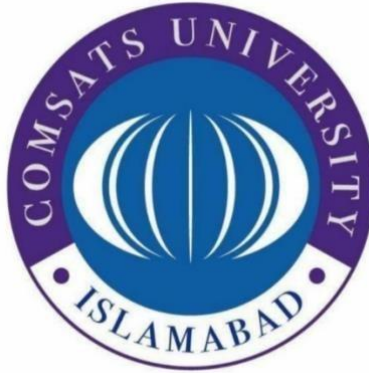


Electric Circuits Analysis

Lab Report # 3



Submitted by:

Haider Ali (FA21-BEE-053)

Muhammad Ahmad (FA21-BEE-095)

Abdul Jalil (FA21-BEE-091)

Submitted To:

Ma'am Rabia Naseem

Lab 03: Experimental Validation of Resistor Combinations - Series and Parallel

Resistance in series

The circuit in which the current remaining parts as before and the voltage is diverse across every resistor is known as an arrangement circuit, as demonstrated in Figure 3.1. In an arrangement circuit the complete obstruction is the amount of individual opposition esteems. On the off chance that k number of resistors is associated in arrangement, the same obstruction R_{eq} is given by,

$$R_{eq} = R_1 + R_2 + R_k$$

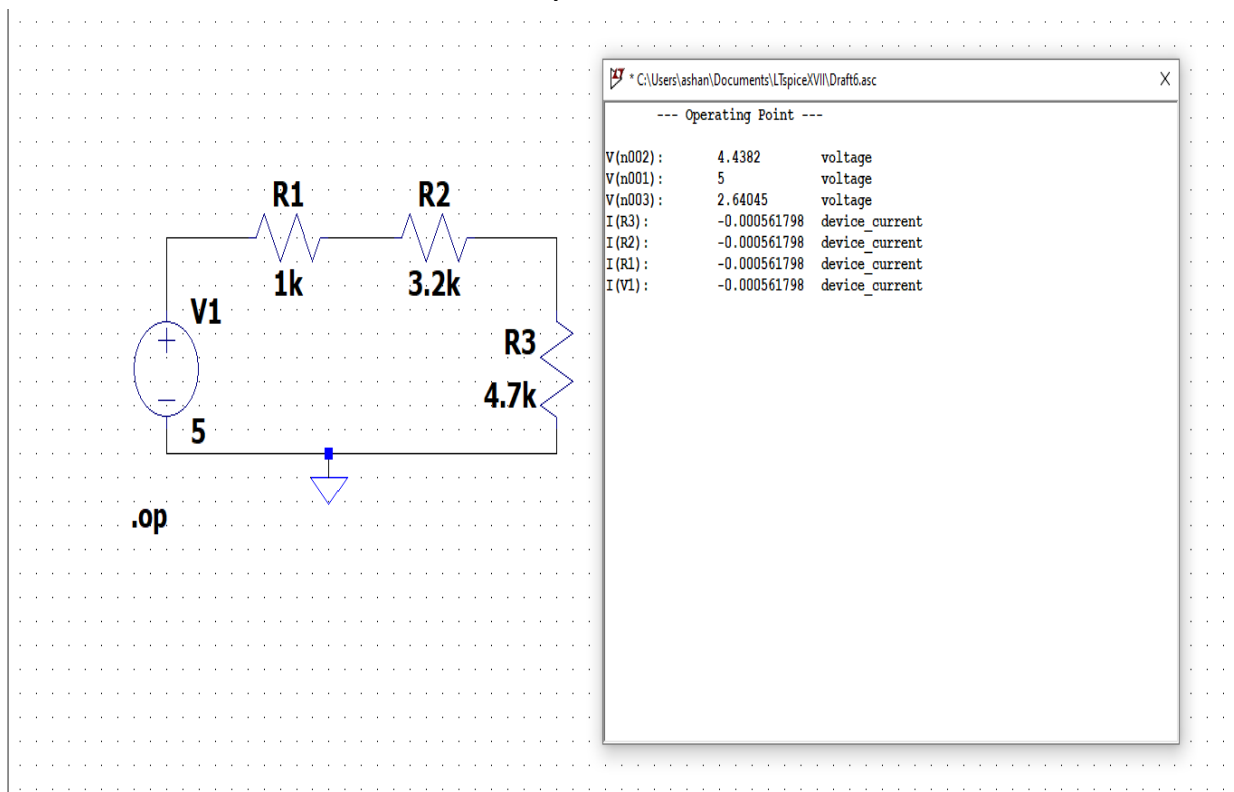


Table 1:

<u>Value of R1 (Ω)</u>	<u>Value of R2 (Ω)</u>	<u>Value of R3 (Ω)</u>	<u>Reqcalculated(Ω)</u>	<u>Reqmeasured(Ω)</u>
1K	3.2k	4.7K	9K	8.78K
<u>iT (mA)</u> <u>calculated</u>	<u>iT (mA)</u> <u>measured</u>	<u>V1 (V) measured</u>	<u>V2 (V) measured</u>	<u>V3 (V) measured</u>
0.556	0.55	0.552	1.823	2.58
<u>iT (mA)</u> <u>Simulated</u>		<u>V1 (V)</u> <u>Simulated</u>	<u>V2 (V)</u> <u>Simulated</u>	<u>V3 (V)</u> <u>Simulated</u>
0.561		0.562	1.798	2.64

Resistances in parallel

In an equal circuit voltage across every one of the resistors stays as before and the inventory current or absolute current is the amount of the individual flows in various equal ways. The amount of the proportional of equal protections associated in the circuit is equivalent to the corresponding of the same obstruction associated in the circuit. On the off chance that k number of resistors is associated in equal, the same opposition Req is given

by, $1/R_{eq} = 1/R_1 + 1/R_2 + 1/R_k$

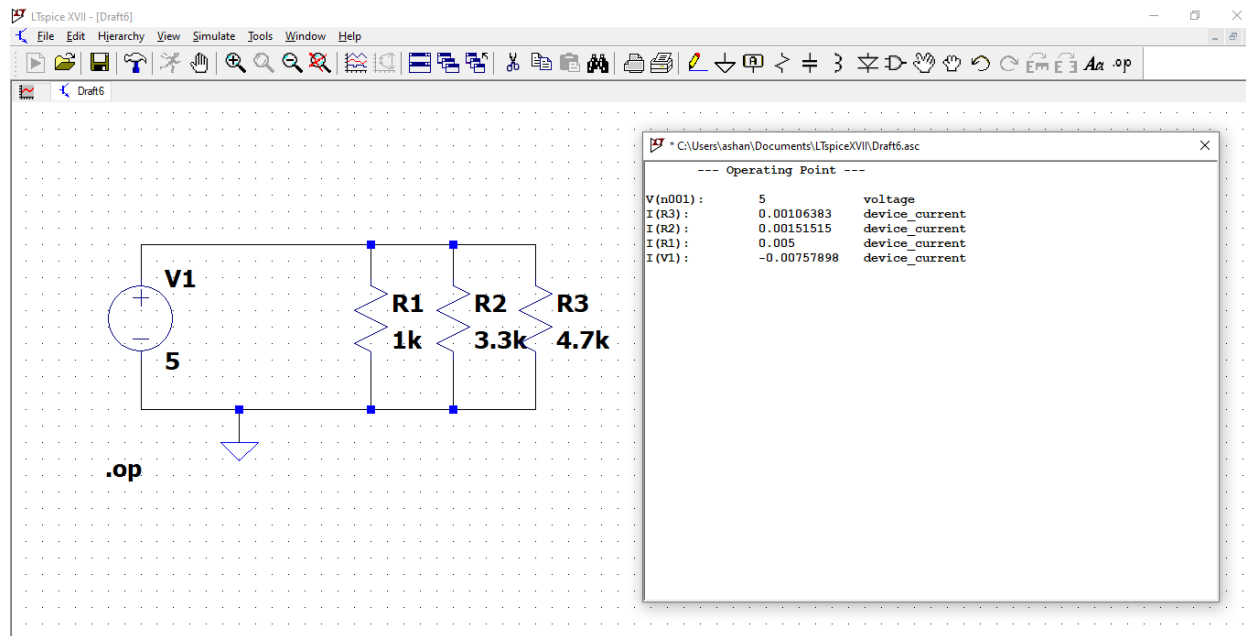


Table 2:

<u>Value of R1</u> <u>(Ω)</u>	<u>Value of R2</u> <u>(Ω)</u>	<u>Value of R3</u> <u>(Ω)</u>	<u>Reqcalculated(Ω)</u>	<u>Reqmeasured(Ω)</u>
1K	3.3K	4.7K	0.6597k	0.656k
<u>iT</u> <u>(mA)calculated</u>	<u>iT</u> <u>(mA)measured</u>	<u>I1</u> <u>(mA)measured</u>	<u>I2 (mA)measured</u>	<u>I3 (mA)measured</u>
7.58	7.32	4.98	1.52	1.07
<u>iT (mA)</u> <u>Simulated</u>		<u>I1 (mA)</u> <u>Simulated</u>	<u>I2 (mA)</u> <u>Simulated</u>	<u>I3 (mA)</u> <u>Simulated</u>
7.5		5	1.51	1.06

Post lab

Questions

1. Assume that you have a $100\ \Omega$ resistor. You want to add a resistor in series with this $100\ \Omega$ resistor in order to limit the current to 0.5 amps when 110 volts is placed across the two resistors in series. How much resistance should you use?

Ans:

$$R_{eq} = 100 + R$$

$$V = 110V \quad I = 0.5\text{amp}$$


$$V = IR \quad ; R_{eq} = V/I$$

$$100 + R = 110/0.5 = 220$$

$$R = 220 - 100$$

$$R = 120\text{ohm}$$

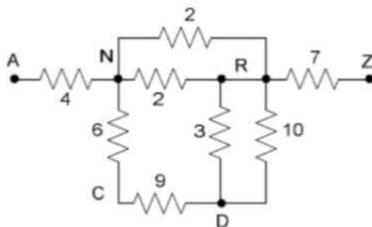2. Identify the resistance pairs that are in parallel in the following circuit:




Ans: 3 and 10 are in parallel making a 2.3ohm resistor

2 and 2 are in parallel making 1ohm resistor

17.3 and 1ohm are in parallel

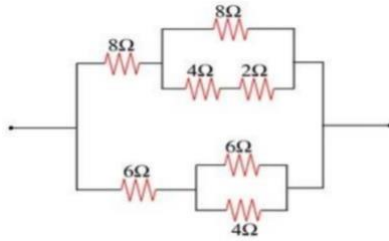3. What is the equivalent resistance of the following resistance combination?



Ans:

Step1: $2+4=6$ (series)

Step2: $6//8= 3.4$ (parallel)

Step3: $8+3.4=11.4$ (series)

Step4: $4//6= 2.4$ (parallel)

Step5: $6+2.4= 8.4$ (series)

Step6: $11.4//8.4=4.8$ (parallel)

Req=4.8ohm

Critical Analysis/Conclusion:

In this lab, we worked with arrangement and equal circuits. In the first place, we utilized resistors of various qualities to ascertain the same obstruction in arrangement, with voltage animated and current also utilizing LTSpice. We played out the equivalent for equal too and noticed the readings. We likewise understood that the current remaining parts same in arrangement while voltage partitions and the other way around for equal circuits.